
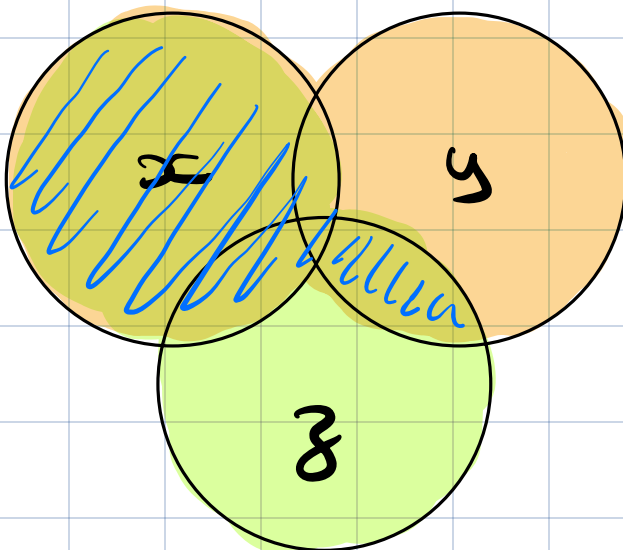



# Exercise 5

a

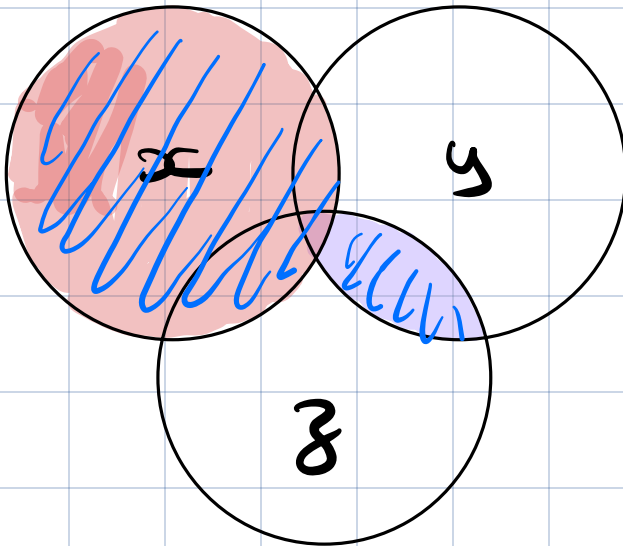


✓

b

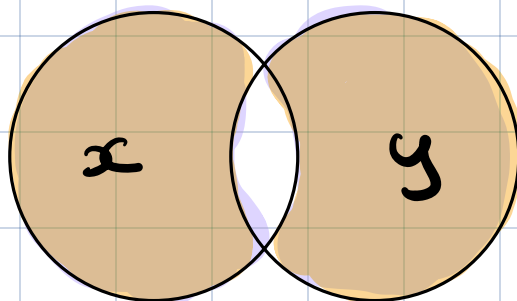

✓

c)

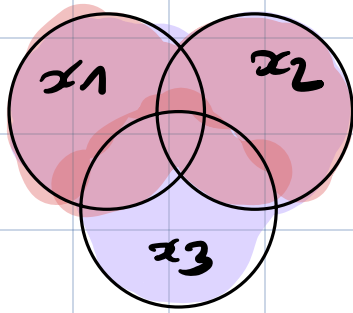

## Exercice 9

$$\textcircled{a} \quad \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}bc + abc + a\bar{b}\bar{c} + abc$$

NOT EQUALS

$$\bar{a}b\bar{c} + \bar{a}bc + \bar{a}bc + abc + a\bar{b}\bar{c} + a\bar{b}\bar{c}$$

$$\textcircled{b} \quad \bar{a}bc + \bar{a}b\bar{c} + \bar{a}bc + \bar{a}bc + \bar{a}bc + \bar{a}bc + \bar{a}bc$$

EQUALS

$$\bar{a}bc + \bar{a}b\bar{c} + \bar{a}bc + \bar{a}bc + \bar{a}bc + \bar{a}bc + \bar{a}bc$$

c)

$$ab\bar{c} + a\bar{b}\bar{c} + abc + \bar{a}bc + abc + a\bar{b}\bar{c} + \bar{a}\bar{b}\bar{c}$$

EQUALS

$$ab + a\bar{c} + \bar{b}\bar{c} + cb$$

①

a  
L |  $ab\bar{c}$

c  
L |  $c\bar{a}$   
 $\bar{a}bc$


a |  $ab\bar{c}$   
 $\bar{a}b$

$\bar{a}bc$   
 $\bar{a}b\bar{c}$  Not  
equals

# Exercise 15


(a)

000	0
001	1
010	2
011	3
100	4
101	5
110	6
111	7

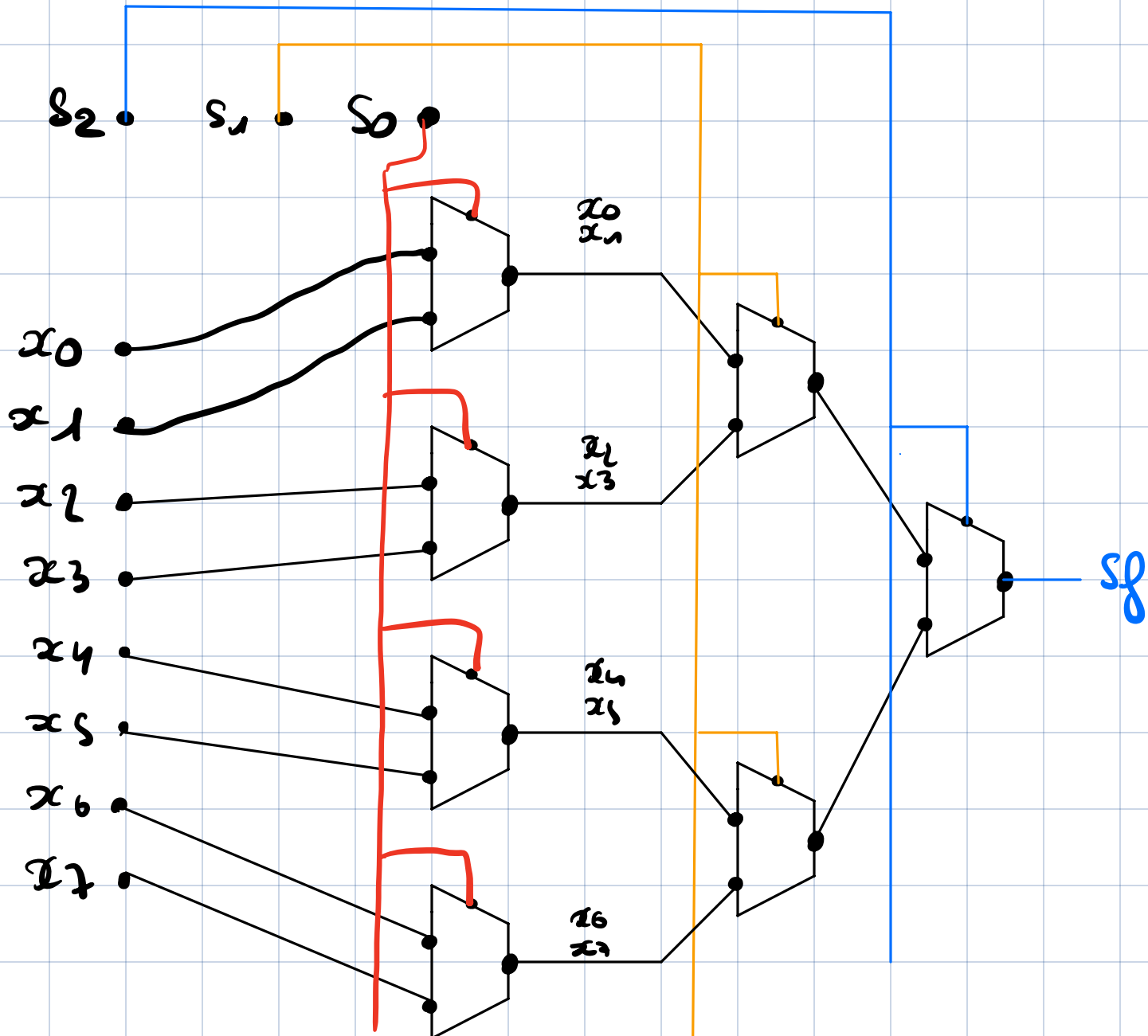

6

000	0
001	1
010	2
011	3
100	4
101	5
110	6
111	7

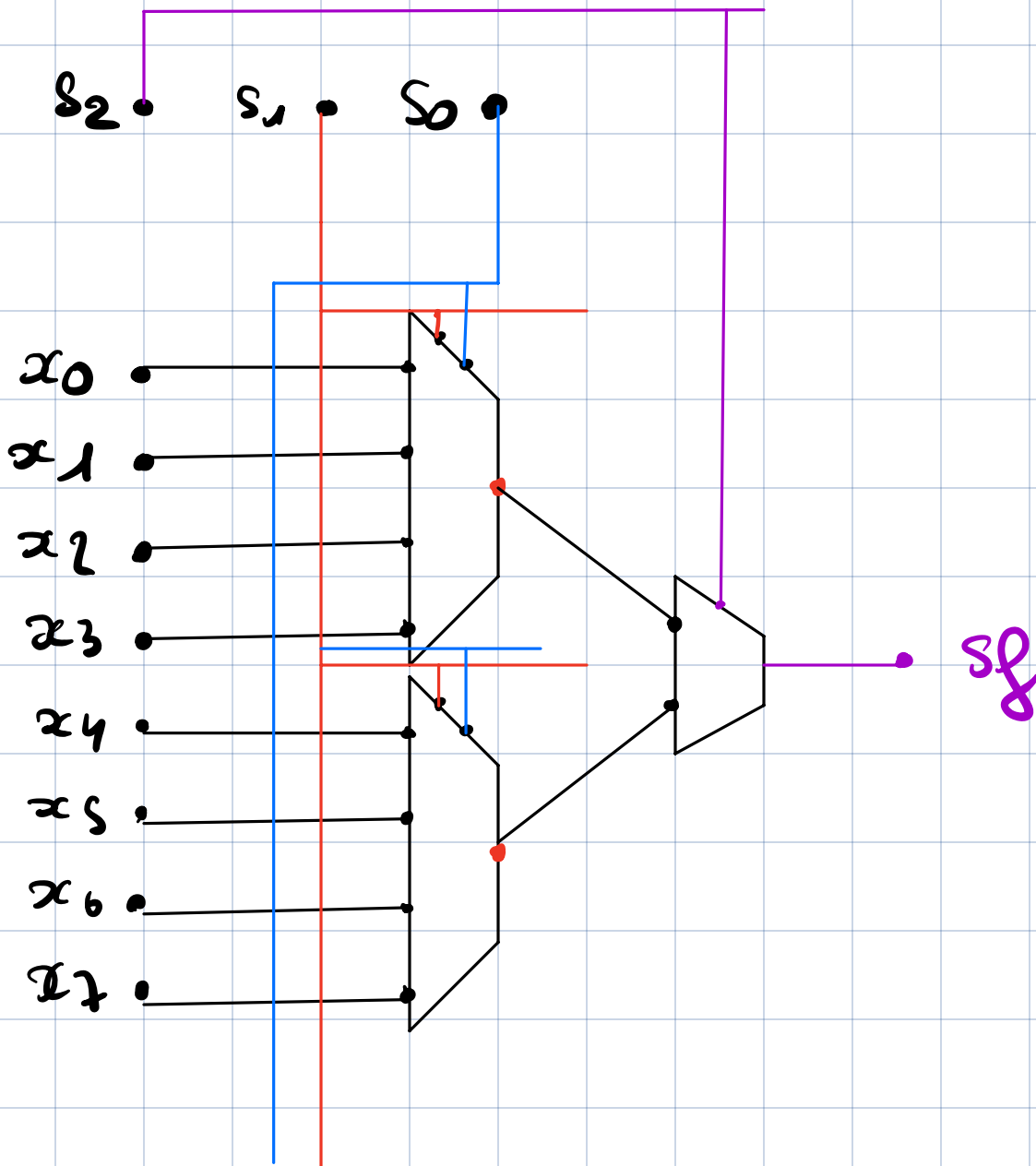

## Exercise 12

i)

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

ii)

$$\begin{aligned} a = & \overline{w} \overline{x} \overline{y} \overline{z} + \overline{w} \overline{x} y \overline{z} \\ & + \overline{w} \overline{x} y z + \overline{w} x \overline{y} z \\ & + \overline{w} x y \overline{z} + \overline{w} x y z \\ & + w \overline{x} \overline{y} \overline{z} + w \overline{x} y z \end{aligned}$$



$$\begin{aligned}
 &= \cancel{\bar{w}\bar{x}\bar{z}} + \bar{w}xz \\
 &+ w\bar{x}\bar{y} + \cancel{\bar{w}\bar{x}yz} \\
 &+ wxy\bar{z}
 \end{aligned}$$


$$= \bar{w}\bar{x} + \bar{w}xz + w\bar{x}\bar{y} + wxy\bar{z}$$

$$\begin{aligned}
 b &= \cancel{\bar{w}\bar{x}\bar{y}\bar{z}} + \cancel{\bar{w}\bar{x}\bar{y}z} + \cancel{\bar{w}\bar{x}y\bar{z}} \\
 &+ \cancel{\bar{w}\bar{x}yz} + \bar{w}x\bar{y}\bar{z} + \bar{w}xy\bar{z} \\
 &+ w\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}z
 \end{aligned}$$


$$\begin{aligned}
 &= \bar{w}\bar{x} + w\bar{x}\bar{y} + \bar{w}x\bar{y}\bar{z} + \bar{w}xy\bar{z} \\
 &= \bar{w}\bar{x} + w\bar{x}\bar{y} + \bar{w}\bar{y}\bar{z} + \bar{w}yz \\
 &= \bar{w}\bar{x} + \bar{x}\bar{y} + \bar{w}\bar{y}\bar{z} + \bar{w}yz
 \end{aligned}$$

# Exercice 17


a

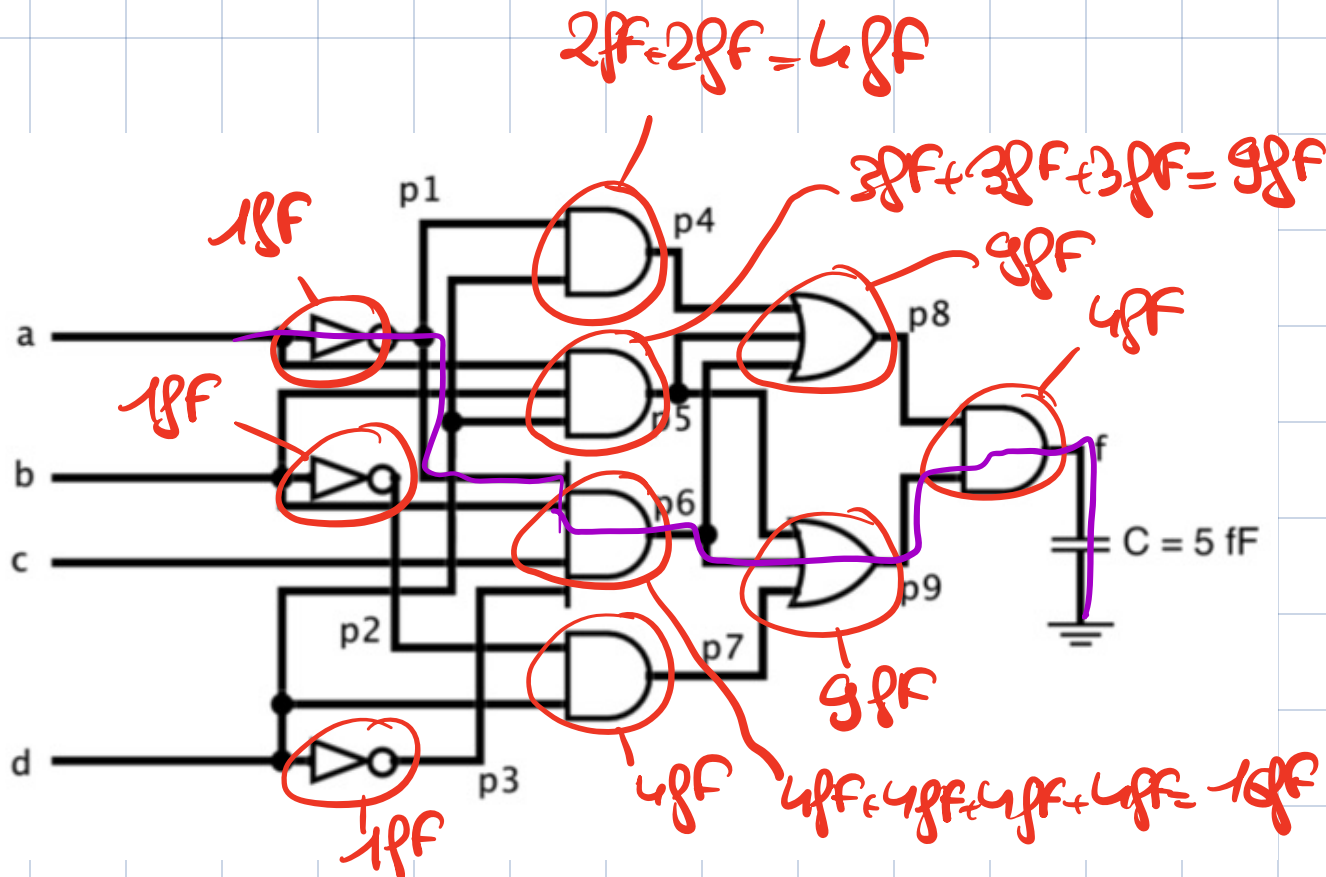

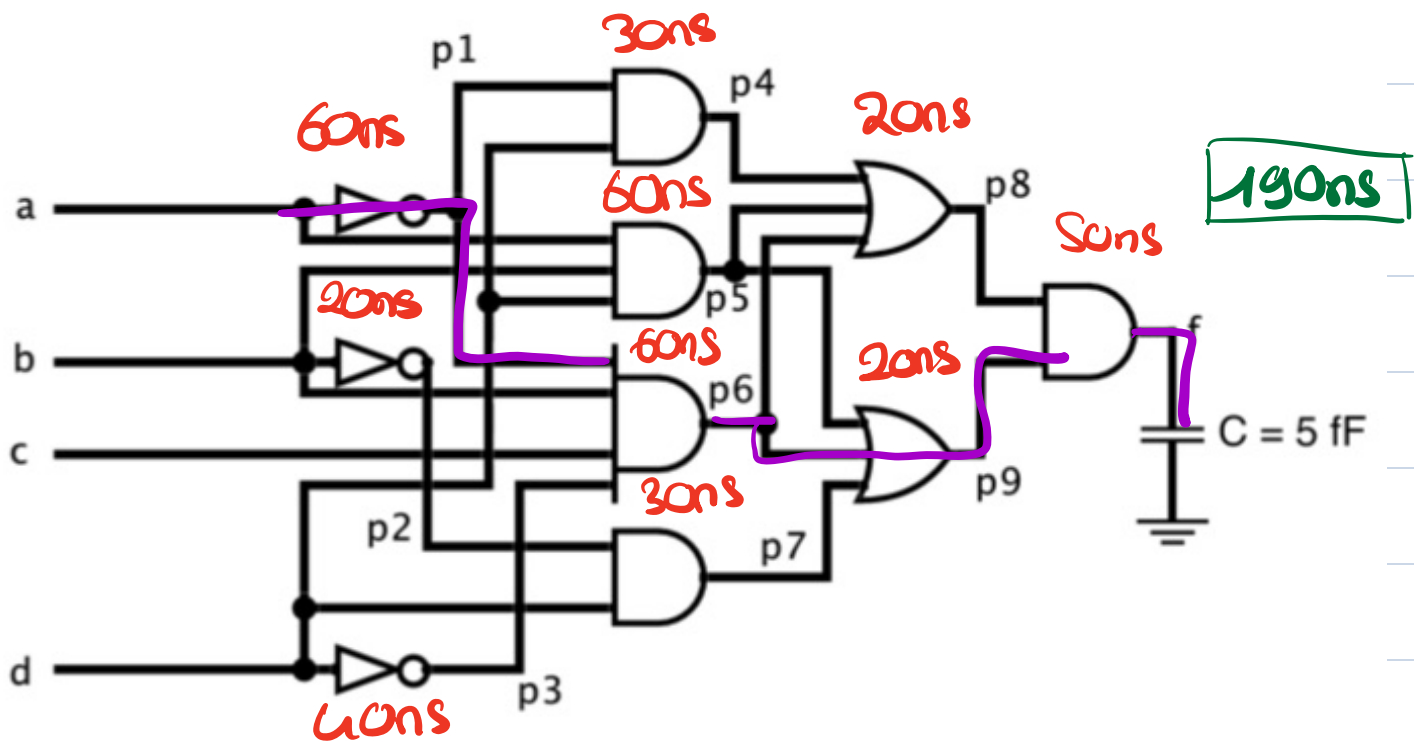pour compter  $\oplus$  simplement, on peut compter uniquement les inputs




Simple logic gate:

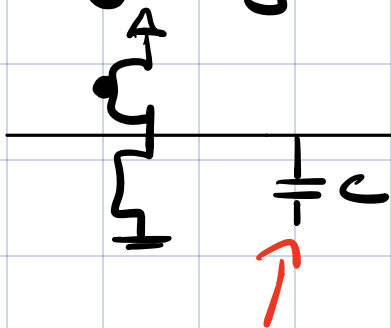

$$C_{in2} = C_{out1}$$

Complex logic gate:

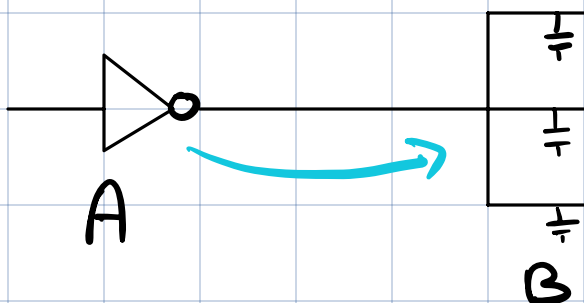

Time it takes for the signal to from A to B depends on how many cap. you need to cross